

Digital Logic

Lab14 Counters & review

Lab14 part1


- Counter
 - Binary counter
 - Johnson counter

Counters

- A counter is essentially a register that goes through a predetermined sequence of binary states. The gates in the counter are connected in such a way as to produce the prescribed sequence of states. Although counters are a special type of register, it is common to differentiate them by giving them a different name.

Binary Counter (1)

 - Synchronous binary counters have a regular pattern



	Present State			Next State		
	Q2	Q1	Q0	D2	D1	D0
s0	0	0	0	0	0	1
s1	0	0	1	0	1	0
s2	0	1	0	0	1	1
s3	0	1	1	1	0	0
s4	1	0	0	1	0	1
s5	1	0	1	1	1	0
s6	1	1	0	1	1	1
s7	1	1	1	0	0	0



Binary Counter (2)

- Design a 3-bits binary counter using algebraic method

```

module count3a(
input wire clr,
input wire clk,
output reg[2:0]Q );
  wire [2:0] D;
  assign D[2] = (Q[1]&Q[0]) ^ Q[2];
  assign D[1] = Q[1]^Q[0];
  assign D[0] = ~Q[0];
  always@(posedge clk or posedge clr)
    if(clr == 1)
      Q<=0;
    else
      Q<=D;
endmodule

```

 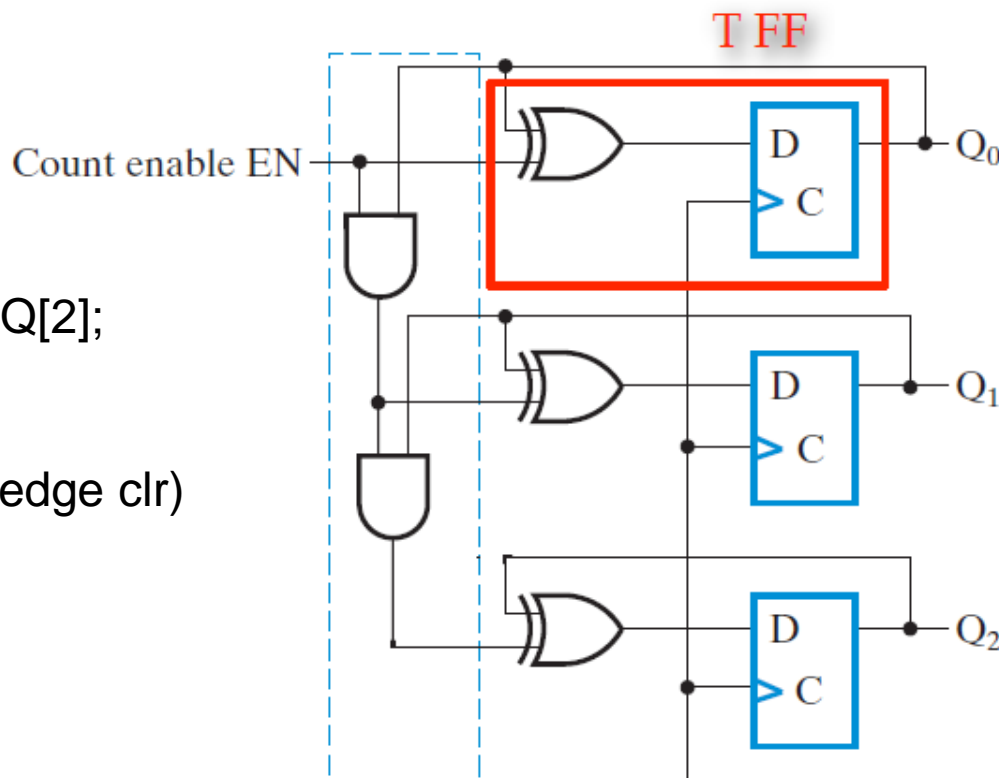


Binary Counter (3)

- Design a 3-bits binary counter using arithmetic method

```

module count3b(
input wire clr,
input wire clk,
output reg[2:0] Q
);
always@(posedge clk or posedge clr)
begin
if(clr == 1)
Q<=0;
else
Q<=Q+1;
end
endmodule

```


 


Johnson-counter(1)

```

module johoson_counter(
input clk,rst_n,output reg [3:0] out):
always @(posedge clk,negedge rst_n) begin
    if(^rst_n)
        out<=4'b0;
    else
        out<={^out[0],out[3:1]};
end
endmodule

```

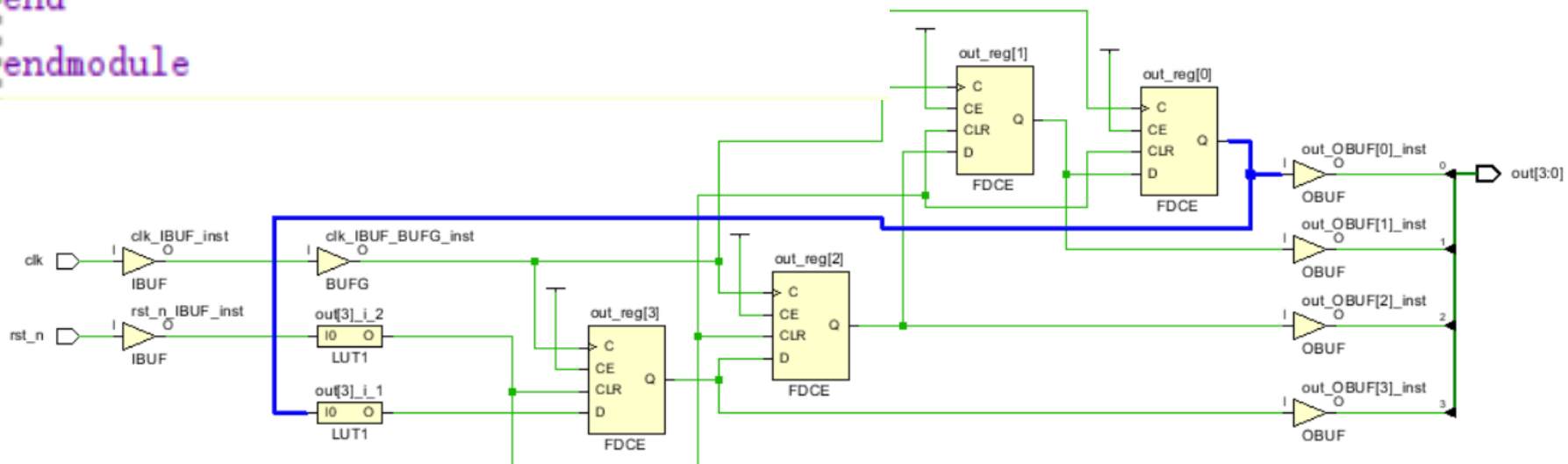 

Johnson-counter(2)

```
module johoson_counter(
input clk,rst_n,output reg [3:0] out);
always @(posedge clk,negedge rst_n) begin
    if(~rst_n)
        out<=4'b0;
    else
        out<={~out[0],out[3:1]};
end
endmodule
```

```
module johnsonCounterTb( );
reg clk,rst_n;
wire [3:0] out;
johoson_counter jc1(clk,rst_n,out);
initial begin
    clk = 1'b0;
    rst_n = 1'b0;
    #3 rst_n = 1'b1;
    forever #5 clk=~clk;
    #160 $finish;
end
endmodule
```

